

ASSIGNMENT 1 – CYCLIC REDUNDANCY CHECK

ARQUITETURA DE ALTO DESEMPENHO

WORK DONE BY:
BERNARDO MARÇAL - 103236
SEBASTIAN GONZALEZ - 103690

PARALLEL ENCODER



$$\begin{aligned} & \left(\sum_{n=0}^{15} a_n \times x^{n+8} \right) \bmod (x^8 + x^7 + x^3 + x^2 + x + 1) = \\ &= (a_0 \oplus a_1 \oplus a_3 \oplus a_5 \oplus a_7 \oplus a_{12} \oplus a_{13}) \times x^7 + \\ &+ (a_1 \oplus a_2 \oplus a_3 \oplus a_4 \oplus a_5 \oplus a_6 \oplus a_7 \oplus a_{11} \oplus a_{13} \oplus a_{15}) \times x^6 + \\ &+ (a_0 \oplus a_1 \oplus a_2 \oplus a_3 \oplus a_4 \oplus a_5 \oplus a_6 \oplus a_{10} \oplus a_{12} \oplus a_{14}) \times x^5 + \\ &+ (a_2 \oplus a_4 \oplus a_7 \oplus a_9 \oplus a_{11} \oplus a_{12} \oplus a_{15}) \times x^4 + \\ &+ (a_1 \oplus a_3 \oplus a_6 \oplus a_8 \oplus a_{10} \oplus a_{11} \oplus a_{14}) \times x^3 + \\ &+ (a_0 \oplus a_2 \oplus a_5 \oplus a_7 \oplus a_9 \oplus a_{10} \oplus a_{13}) \times x^2 + \\ &+ (a_0 \oplus a_3 \oplus a_4 \oplus a_5 \oplus a_6 \oplus a_7 \oplus a_8 \oplus a_9 \oplus a_{13} \oplus a_{15}) \times x + \\ &+ (a_0 \oplus a_1 \oplus a_2 \oplus a_4 \oplus a_6 \oplus a_8 \oplus a_{13} \oplus a_{14}) \end{aligned}$$

- 58 x-or gates are needed

To get the result we expected, we used the **Property of the Reminder**, and while doing this we tried to reduce the number of XORs the most we could so we reduce the time delays

[illegible]


ENCODER ARCHITECTURE

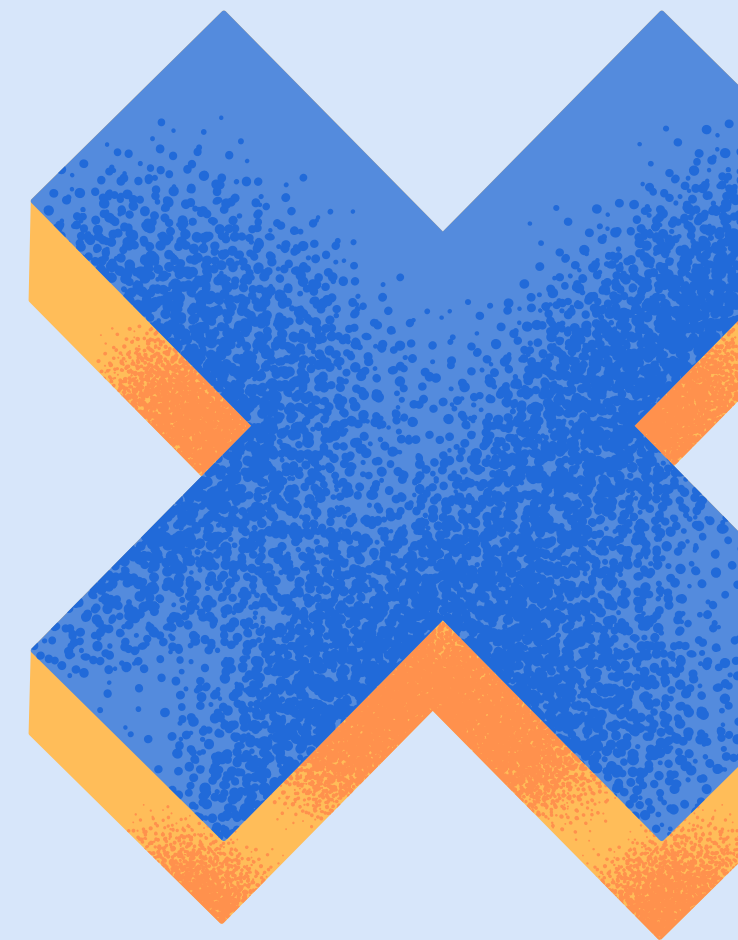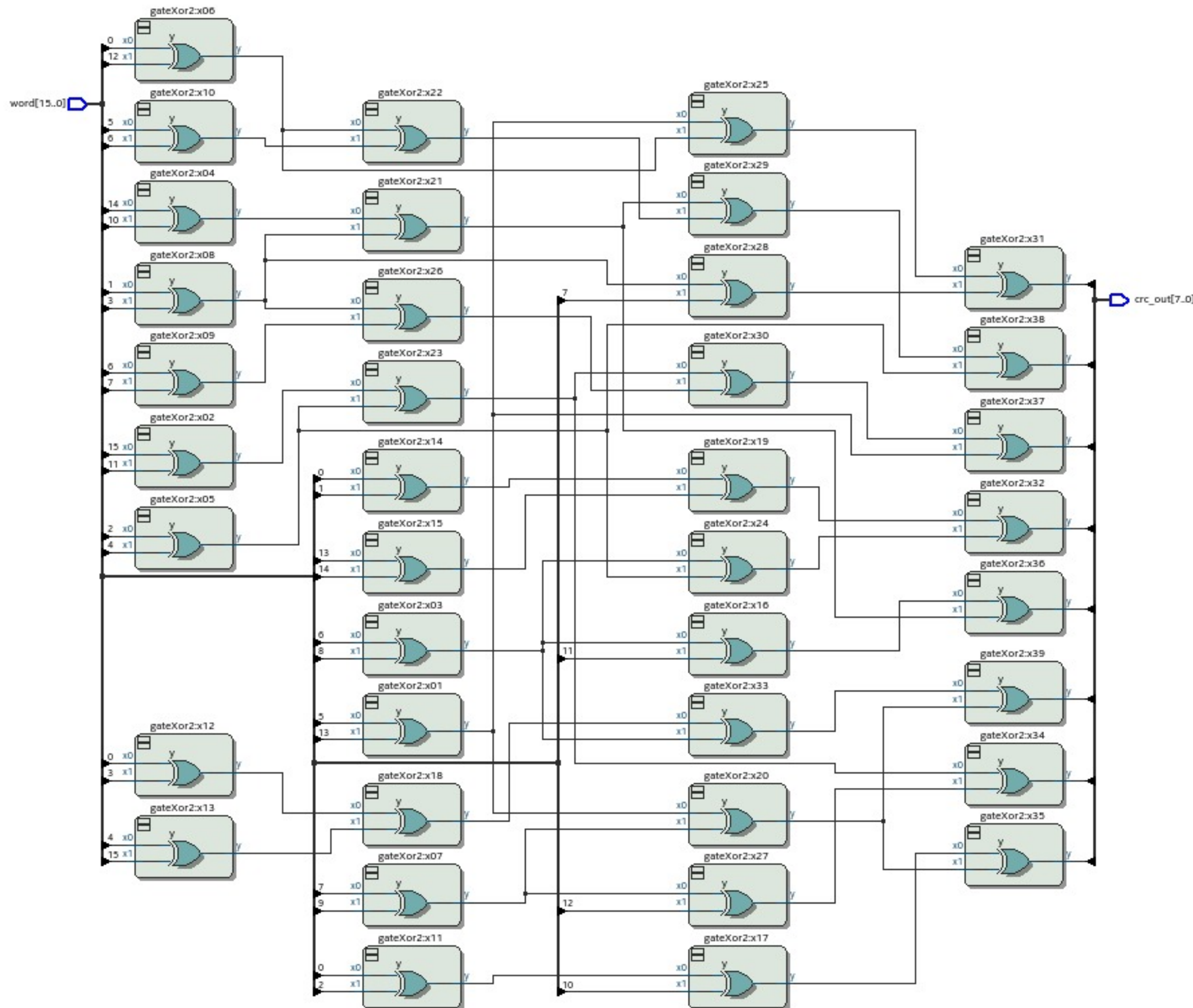

**39 Total
XORs**

**4 Propagation
Time Delay**

BIT-SERIAL CHECKER

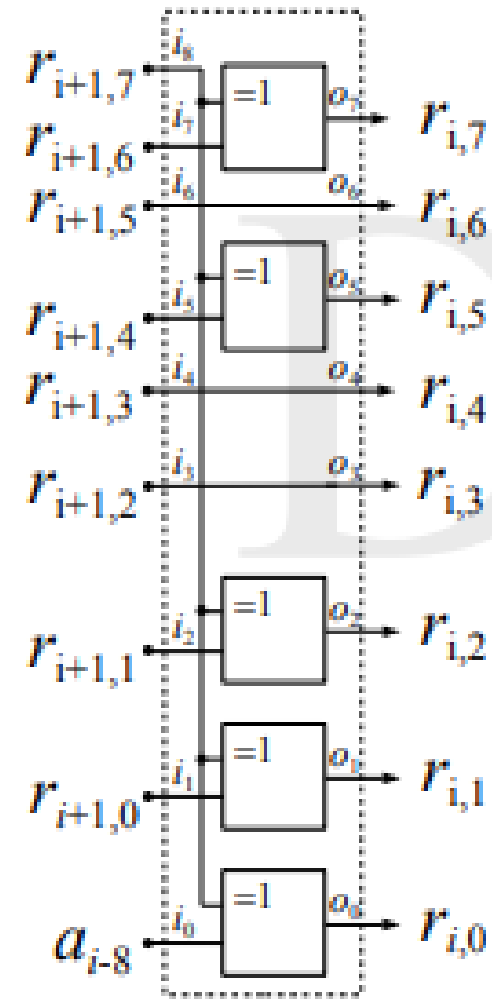

building block of type 1
9 inputs

